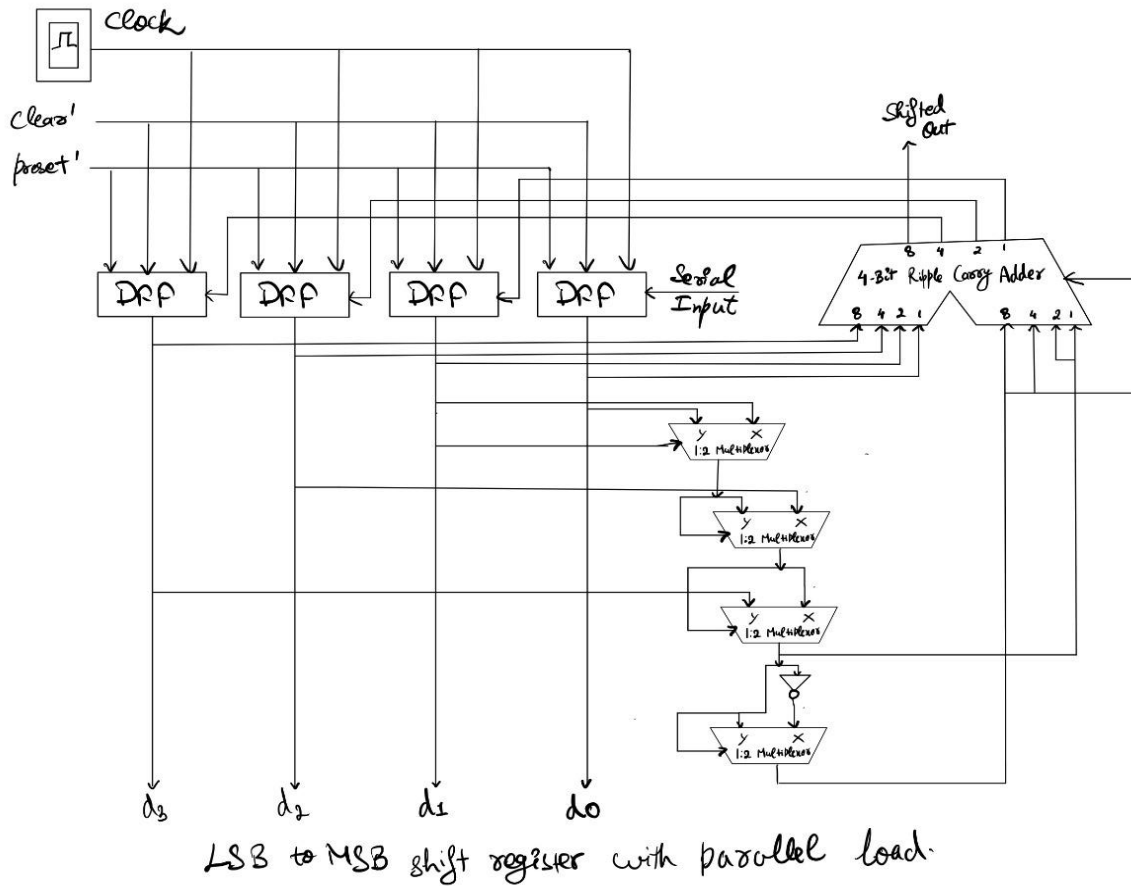


EXPERIMENT 06

SEQUENTIAL DOUBE-DABBLE

SHIFT REGISTER WITH PARALLEL LOAD



This is a shift register that shifts from *LSB* to *MSB*. This shift register is responsible in performing the most crucial step of *double-dabble algorithm* -- *ADD 3* and *SHIFT LEFT*. The component does both the steps simultaneously.

This shift register handles a single nibble (4 bits). To be able to construct the logic for a complete *binary to BCD converter*, several *shift registers* might need to be connected in cascade. This realization is discussed in the next section.

Observe the four bits d_3 , d_2 , d_1 and d_0 shown in the output. The values of these bits change at every *negative/falling edge* of the clock pulse. Two operations happen when the falling edge of the clock is witnessed.

- *ADD 3* which is the characteristic induced by the parallel circuitry that basically acts as a *>4 conditional 3 adder*.
- *SHIFT LEFT* which is the intrinsic characteristic of an *LSB to MSB shift register*. *SHIFT LEFT* operation not only shifts the present nibble $d_3d_2d_1d_0$ in the output towards the left in order to push the *leading bit* d_3 out, but also simultaneously receives a new bit i from the *serial stream of input bits* to display the nibble $d_2d_1d_0i$ in the output.

Observe that these two operations are the core of the *double-dabble algorithm*. The algorithm is made up of alternately applying two operations *ADD 3* and *LEFT SHIFT*. While the former operation is conditional, the latter must be applied after every one step.

One first checks the decimal value of each of the *nibbles* in the *current intermediate BCD output* starting from the *least significant bit*. If any such nibble has a decimal value of *greater than 4*, *binary 3* (0011) is added to it. After this, the very next step is the *LEFT SHIFT* in which the *next bit* from the *binary input string* is taken in.

Since the *ADD 3* operation involves checking groups of 4 bits and conditionally adding 3 to them, the *shift register* we have designed in this section is the one that takes 4 inputs.

Note that the *parallel load* that acts as a *>4 conditional 3 adder* is designed by *multiplexors* using *Shannon's decomposition* on the boolean function that was used in implementing the *first part of experiment 2*. Addition of two 4-bit binary strings is done using a *ripple carry adder*.

The simulation of the above circuit diagram can be illustrated in the following way.

Since in this experiment we are dealing only with 7 bit binary strings, let the input stream consist of the 7 bits $d_7 d_6 d_5 d_4 d_3 d_2 d_1$.

Set the *clear'* input to 0 (*preset'* will remain one) to *clear* the bits being initially displayed in the output. Start the clock, wait until one falling edge is completely witnessed. The output bits are now cleared (similar to *initialization step* in *double-dabble algorithm*). Set *clear'* input to 1 and restart the clock. The working of the above circuit for a general 7 bit input binary string can be understood as follows.

<i>Falling Edge Index</i>	<i>Operation the shift register is performing</i>	<i>Current Output Nibble</i>	<i>Next Bit in the Stream</i>
0	<i>INITIALIZATION</i>	0000	d_7
1	<i>ADD 3</i>	0000	d_7
1	<i>SHIFT LEFT</i>	$000d_7$	d_6
2	<i>ADD 3</i>	$000d_7$	d_6
2	<i>SHIFT LEFT</i>	$00d_7d_6$	d_5
3	<i>ADD 3</i>	$00d_7d_6$	d_5
3	<i>SHIFT LEFT</i>	$0d_7d_6d_5$	d_4
4	<i>ADD 3</i>	$e_4e_3e_2e_1$	d_4
4	<i>SHIFT LEFT</i>	$e_3e_2e_1d_4$	d_3
5	<i>ADD 3</i>	$f_4f_3f_2f_1$	d_3

5	<i>SHIFT LEFT</i>	$f_3 f_2 f_1 d_3$	d_2
6	<i>ADD 3</i>	$g_4 g_3 g_2 g_1$	d_2
6	<i>SHIFT LEFT</i>	$g_3 g_2 g_1 d_2$	d_1
7	<i>ADD 3</i>	$h_4 h_3 h_2 h_1$	d_1
7	<i>SHIFT LEFT</i>	$h_3 h_2 h_1 d_1$	—

(NOTE: In the first three ADD 3 operations, the output nibble will definitely not change because a 4 bit binary string with the two most significant bits as 0 can never be greater than 4 in decimal.

This is a simulation for a general input. There might be other ADD 3 operations too where the output nibble stays intact.)

The simulation signifies that the clock must completely witness 7 falling edges in order to reach the end of the simulated algorithm. So *stop the clock after 7 falling edges are seen.*

The same circuit diagram was implemented as follows.

As was subtly mentioned in the last section, the *shift registers* can be cascaded in order to realize a *7 bit binary to BCD converter*. In this cascade design, the *shifted out* bit of one register is the *serial input* of the other register. The *operations (ADD 3 and LEFT SHIFT)* of all the three registers are *synchronized* because they are connected to the same clock.


First of all, in the design exactly three registers were taken because the *BCD representation* of a 7 bit binary string can have at most 12 bits (3 nibbles); therefore one register is needed to deal with each of the nibbles. The working of this circuit diagram is exactly the same as the shift register itself (as was discussed in the last section), excluding the fact that though the rightmost shift register receives its input bit from the *serial stream of input bits*, for the other two registers, the input bit is the output bit of the register on the right.

So each of the three registers have there own *input streams* and a *similar simulation chart* can be drawn for each one of them.

As in the last section the clock must completely witness 7 falling edges in order to reach the end of the simulated algorithm. So *stop the clock after 7 falling edges are seen. It is at this point that the three output nibbles represent the BCD representation of the 7 bit binary string.*

(The *initialization step* of initially setting *clear* as 0 is the same as before)

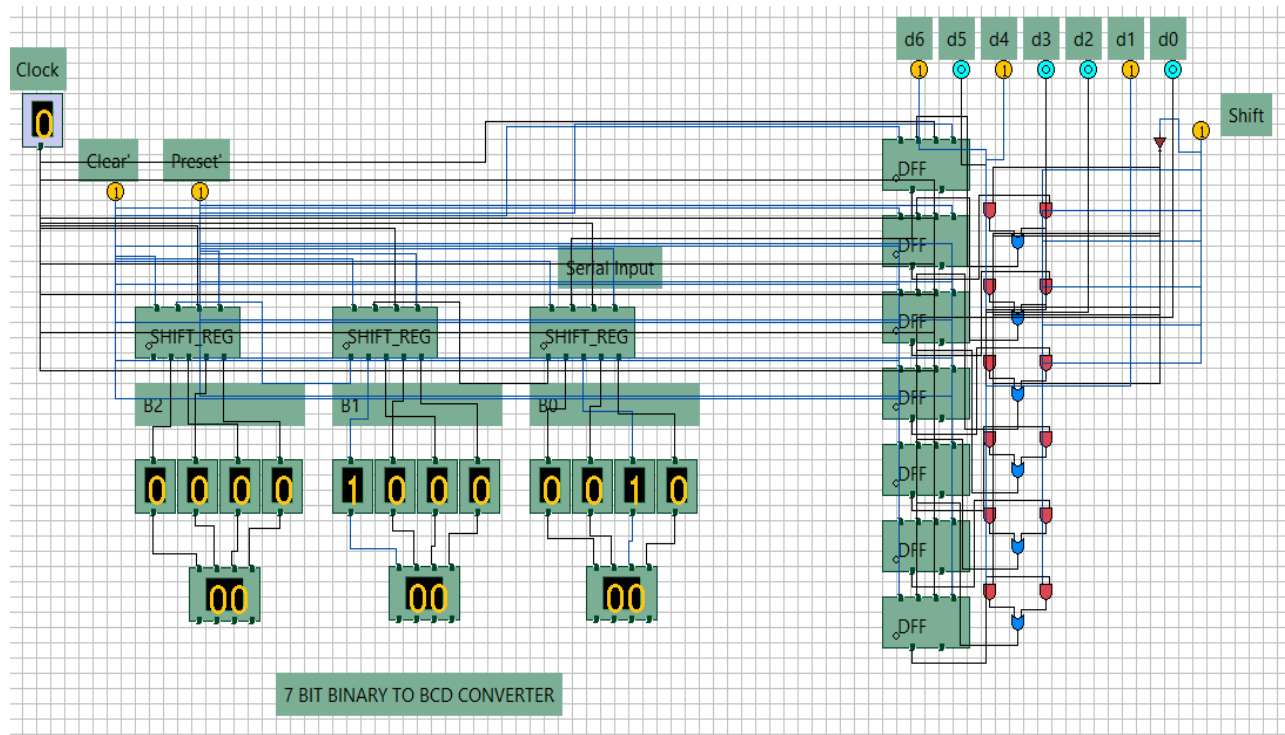The above circuit diagram was implemented as follows.



How is the 7 bit binary string given altogether converted into a serial stream of bits?

For this we need a similar shift register. This register should also shift from *LSB* to *MSB*. We cannot use the shift register we designed in the first section because *it has a parallel circuitry to handle conditional addition of binary 3*. We do not want this while converting a *binary string* into a *bit stream* because it can corrupt/modify the original bits. Therefore, a simple *parallel-in serial-out (PISO)* register is designed (*see the right extreme*) that is also synchronized with the other registers by being connected to the same clock. It *shifts out* each bit in the input binary string (from the *MSB*) one by one, whenever a falling edge is encountered in the clock. To enable shifting, the *shift* input parameter must be set to 1. In the initialization step, the *shift* parameter must be first set to 0 (with *clear'* obviously equal to 1) to enable *loading* of the 7 bit binary string and *latching* of data in the *D flip flops*.

Since here we have used the same *clear'* parameter for both the sub-units, you should first set *clear'* to 0 and clear all the output bits. Then you should set *clear'* to 1 and *shift* to 0 to *load* data. Then *shift* must also be set to 1 to start the simulation.